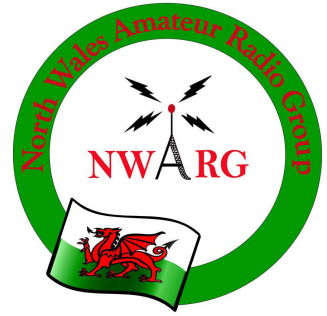


Brass Tacks

An in-depth look at Crystal Oscillators with MW0JWP



Crystal Oscillators:


One of the most important features of any oscillator is its frequency stability, or in other words its ability to provide a constant frequency output under varying load conditions.

Quartz crystal oscillators overcome some of the factors that affect the frequency stability of an oscillator. These generally include: variations in temperature, variations in the load, as well as changes to its DC power supply voltage to name a few.

Frequency stability of the output signal can be greatly improved by the proper selection of the components used for the resonant feedback circuit, including the amplifier. But there is a limit to the stability that can be obtained from normal LC and RC tank circuits.


To obtain a very high level of oscillator stability a Quartz Crystal is generally used as the frequency determining device to produce another types of oscillator circuit known generally as a Quartz Crystal Oscillator, (XO).

When a voltage source is applied to a small thin piece of quartz crystal, it begins to change shape producing a characteristic known as the Piezo-electric effect. This Piezo-electric Effect is the property of a crystal by which an electrical charge produces a mechanical force by changing the shape of the crystal and vice versa, a mechanical force applied to the crystal produces an electrical charge.

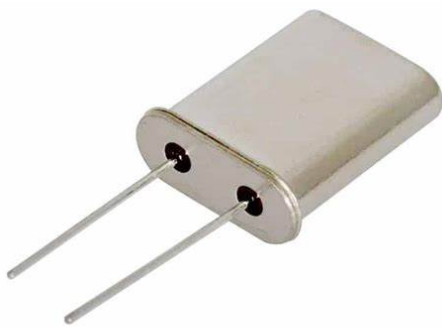

Then, piezo-electric devices can be classed as Transducers as they convert energy of one kind into energy of another (electrical to mechanical or mechanical to electrical). This piezo-electric effect produces mechanical vibrations or oscillations which can be used to replace the standard LC tank circuit in the previous oscillators.

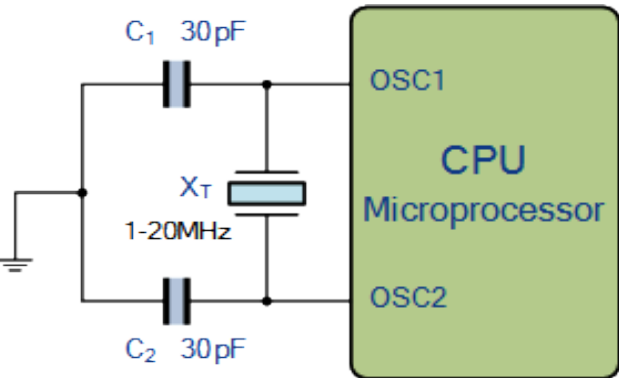There are many different types of crystal substances that can be used as oscillators with the most important of these for electronic circuits being the quartz minerals, due in part to their greater mechanical strength.



Crystal Oscillators with MW0JWP

Brass Tacks


continued



The quartz crystal used in a Quartz Crystal Oscillator is a very small, thin piece or wafer of cut quartz with the two parallel surfaces metallised to make the required electrical connections. The physical size and thickness of a piece of quartz crystal is tightly controlled since it affects the final or fundamental frequency of oscillations. The fundamental frequency is generally called the crystals "characteristic frequency".

Once cut and shaped, the crystal can not be used at any other frequency. In other words, its size and shape determines its fundamental oscillation frequency.

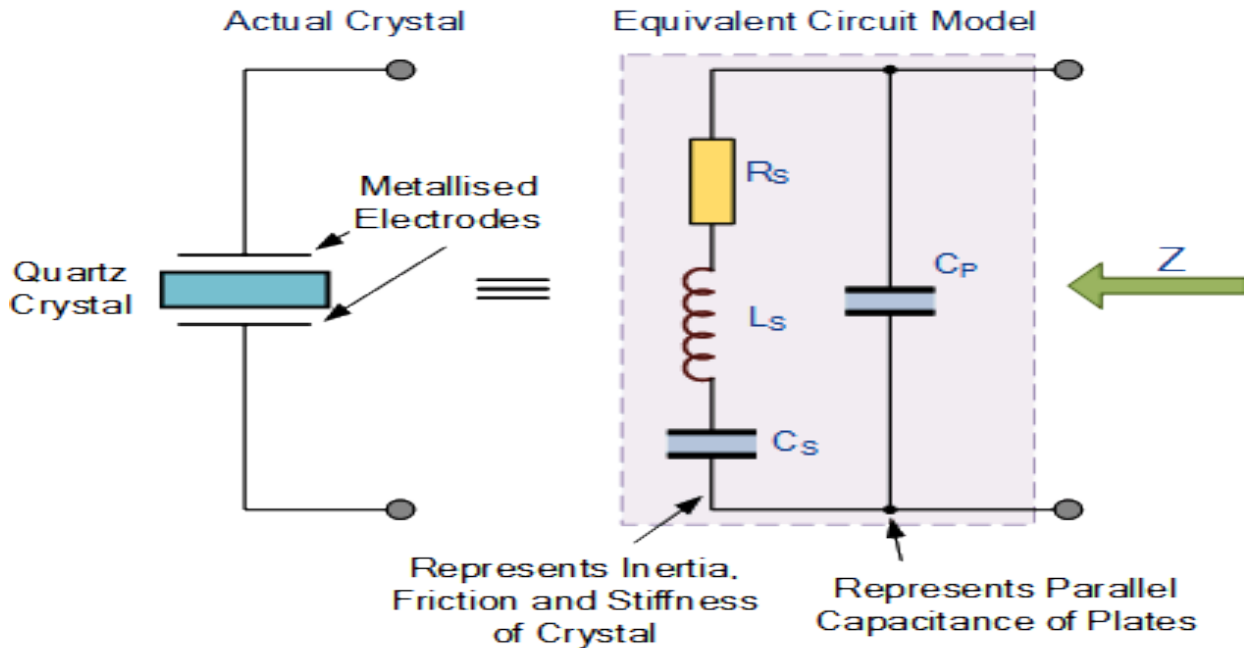The crystals characteristic or characteristic frequency is inversely proportional to its physical thickness between the two metallised surfaces. A mechanically vibrating crystal can be represented by an equivalent electrical circuit consisting of low resistance R , a large inductance L and small capacitance C as shown below.



The equivalent electrical circuit for the quartz crystal shows a series RLC circuit, which represents the mechanical vibrations of the crystal, in parallel with a capacitance, C_p which represents the electrical connections to the crystal. Quartz crystal oscillators tend to operate towards their "series resonance".

The equivalent impedance of the crystal has a series resonance where C_s resonates with inductance, L_s at the crystals operating frequency. This frequency is called the crystals series frequency, f_s . As well as this series frequency, there is a second frequency point established as a result of the parallel resonance created when L_s and C_s resonates with the parallel capacitor C_p as shown..

Brass Tacks

continued



Crystal Impedance against Frequency

$$R = R \quad \text{and} \quad X_{LS} = 2\pi f L_S$$

$$X_{CS} = \frac{1}{2\pi f C_S} \quad \text{and} \quad X_{CP} = \frac{1}{2\pi f C_P}$$

$$Z_S = \sqrt{R_S^2 + (X_{LS} - X_{CS})^2}$$

$$\therefore Z_P = \frac{Z_S \times X_{CP}}{Z_S + X_{CP}}$$


The slope of the crystals impedance above shows that as the frequency increases across its terminals. At a particular frequency, the interaction of between the series capacitor C_S and the inductor L_S creates a series resonance circuit reducing the crystals impedance to a minimum and equal to R_S . This frequency point is called the crystals series resonant frequency f_S and below f_S the crystal is capacitive.

As the frequency increases above this series resonance point, the crystal behaves like an inductor until the frequency reaches its parallel resonant frequency f_P . At this frequency point the interaction between the series inductor, L_S and parallel capacitor, C_P creates a parallel tuned LC tank circuit and as such the impedance across the crystal reaches its maximum value.

Then we can see that a quartz crystal is a combination of a series and parallel tuned resonance circuits, oscillating at two different frequencies with the very small difference between the two depending upon the cut of the crystal. Also, since the crystal can operate at either its series or parallel resonance frequencies, a crystal oscillator circuit needs to be tuned to one or the other frequency as you cannot use both together.

So depending upon the circuit characteristics, a quartz crystal can act as either a capacitor, an inductor, a series resonance circuit or as a parallel resonance circuit and to demonstrate this more clearly, we can also plot the crystals reactance against frequency as shown.

Crystal Reactance against Frequency

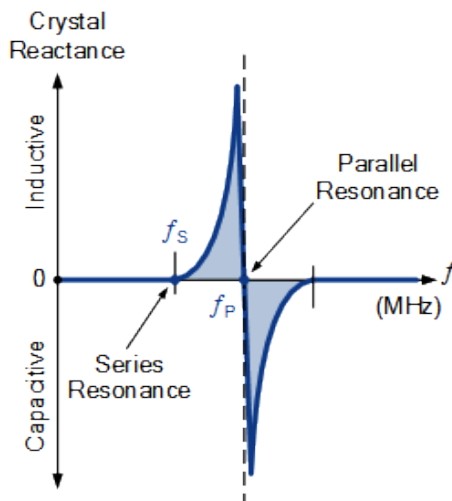

$$X_S = R^2 + (X_{LS} - X_{CS})^2$$

$$X_{CP} = \frac{-1}{2\pi f C_P}$$

$$X_P = \frac{X_S \times X_{CP}}{X_S + X_{CP}}$$

Brass Tacks

continued



The slope of the reactance against frequency above, shows that the series reactance at frequency f_s is inversely proportional to C_s because below f_s and above f_p the crystal appears capacitive. Between frequencies f_s and f_p , the crystal appears inductive as the two parallel capacitances cancel out.

Then the formula for the crystals series resonance frequency, f_s is given as:

$$f_s = \frac{1}{2\pi\sqrt{L_s C_s}}$$

The parallel resonance frequency, f_p occurs when the reactance of the series LC leg equals the reactance of the parallel capacitor, C_p and is given as:

$$f_p = \frac{1}{2\pi\sqrt{L_s \left(\frac{C_p C_s}{C_p + C_s} \right)}}$$

Quartz Crystal Oscillator Example No1

A quartz crystal has the following values: $R_s = 6.4 \Omega$, $C_s = 0.09972\text{pF}$ and $L_s = 2.546\text{mH}$. If the capacitance across its terminal, C_p is measured at 28.68pF , Calculate the fundamental oscillating frequency of the crystal and its secondary resonance frequency.

The crystals series resonant frequency, f_s

$$f_s = \frac{1}{2\pi\sqrt{L_s C_s}} = \frac{1}{2\pi\sqrt{2.546\text{mH} \times 0.09972\text{pF}}}$$

$$f_s = \frac{1}{2\pi\sqrt{0.002546 \times 99.72 \times 10^{-15}}} = 9.987\text{MHz}$$

Brass Tacks

continued



The crystal's parallel resonant frequency, f_p

$$f_p = \frac{1}{2\pi \sqrt{L_s \left(\frac{C_p C_s}{C_p + C_s} \right)}}$$

$$f_p = \frac{1}{2\pi \sqrt{2.546\text{mH} \left(\frac{28.68\text{pF} \times 0.09972\text{pF}}{28.68\text{pF} + 0.09972\text{pF}} \right)}}$$

$$f_p = 10,004,996\text{Hz or } 10.005\text{MHz}$$

We can see that the difference between f_s , the crystal's fundamental frequency and f_p is small at about 18kHz (10.005MHz - 9.987MHz). However during this frequency range, the Q-factor (Quality Factor) of the crystal is extremely high because the inductance of the crystal is much higher than its capacitive or resistive values. The Q-factor of our crystal at the series resonance frequency is given as:

Crystal Oscillators Q-factor:

$$Q = \frac{X_L}{R} = \frac{2\pi f L}{R} = \frac{2\pi \times 9.987 \times 10^6 \times 0.002546}{6.4}$$

$$Q = 24966 \text{ or } 25,000$$

Then the Q-factor of our crystal example, about 25,000, is because of this high X_L/R ratio. The Q-factor of most crystals is in the area of 20,000 to 200,000 as compared to a good LC tuned tank circuit we looked at earlier which will be much less than 1,000. This high Q-factor value also contributes to a greater frequency stability of the crystal at its operating frequency making it ideal to construct crystal oscillator circuits.

Brass Tacks

continued



So we have seen that a quartz crystal has a resonant frequency similar to that of an electrically tuned LC tank circuit but with a much higher Q factor. This is due mainly to its low series resistance, R_s . As a result, quartz crystals make an excellent component choice for use in oscillators especially very high frequency oscillators.


Typical crystal oscillators can range in oscillation frequencies from about 40kHz to well over 100MHz depending upon their circuit configuration and the amplifying device used. The cut of the crystal also determines how it will behave as some crystals will vibrate at more than one frequency, producing additional oscillations called overtones.

Also, if the crystal is not of a parallel or uniform thickness it may have two or more resonant frequencies both with a fundamental frequency producing what are called and harmonics, such as second or third harmonics.

Generally though the fundamental oscillating frequency for a quartz crystal is much more stronger or pronounced than that of and secondary harmonics around it so this would be the one used. We have seen in the graphs above that a crystals equivalent circuit has three reactive components, two capacitors plus an inductor so there are two resonant frequencies, the lowest is a series resonant frequency and the highest is the parallel resonant frequency.

We have seen in the previous tutorials, that an amplifier circuit will oscillate if it has a loop gain greater or equal to one and the feedback is positive. In a Quartz Crystal Oscillator circuit the oscillator will oscillate at the crystals fundamental parallel resonant frequency as the crystal always wants to oscillate when a voltage source is applied to it.

However, it is also possible to "tune" a crystal oscillator to any even harmonic of the fundamental frequency, (2nd, 4th, 8th etc.) and these are known generally as Harmonic Oscillators while Overtone Oscillators vibrate at odd multiples of the fundamental frequency, (3rd, 5th, 11th etc). Generally, crystal oscillators that operate at overtone frequencies do so using their series resonant frequency.

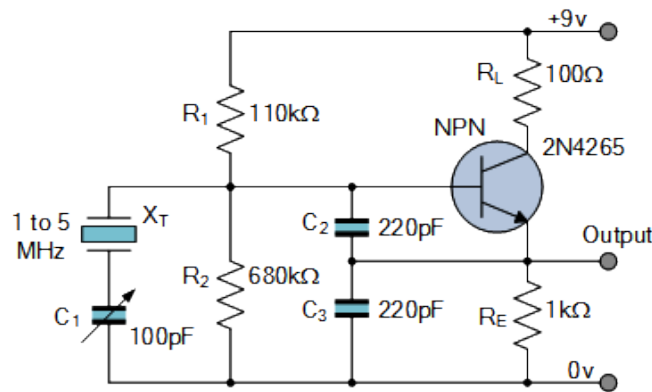

Colpitts Crystal Oscillator